


(a) Block diagram



(b) Timing diagram of clock pulses

Synchronous clocked sequential circuit



The outputs are formed by a combinational logic function of the inputs to the circuit or the values stored in the flip-flops (or both).

The value that is stored in a flip-flop when the clock pulse occurs is also determined by the inputs to the circuit or the values presently stored in the flip-flop (or both).

The new value is stored (i.e., the flip-flop is updated) when a pulse of the clock signal occurs. Prior to the occurrence of the clock pulse, the combinational logic forming the next value of the flip-flop must have reached a stable value.

Consequently, the speed at which the combinational logic circuits operate is critical.


If the clock (synchronizing) pulses arrive at a regular interval, as shown in the timing diagram the combinational logic must respond to a change in the state of the flip-flop in time to be updated before the next pulse arrives.

Propagation delays play an important role in determining the minimum interval between clock pulses that will allow the circuit to operate correctly.


Latches

A **latch** is a temporary storage device that has two stable states (bistable). It is a basic form of memory.

 
The S-R (Set-Reset) latch is the most basic type. It can be constructed from NOR gates or NAND gates. With NOR gates, the latch responds to active-HIGH inputs; with NAND gates, it responds to active-LOW inputs.



NOR Active-HIGH Latch

 

NAND Active-LOW Latch





Storage elements that operate with signal levels (rather than signal transitions) are referred to as latches; those controlled by a clock transition are flip-flops.



Latches are said to be level sensitive devices; flip-flops are edge-sensitive devices.

The two types of storage elements are related because latches are the basic circuits from which all flip-flops are constructed.

  
Although latches are useful for storing binary information and for the design of asynchronous sequential circuits, they are not practical for use as storage elements in synchronous sequential circuits.



  
(a) Two possibilities for the SET operation



 
(b) Two possibilities for the RESET operation



(c) No-change condition

 

(d) Invalid condition



When both inputs are low at once, however, there is a problem: it is being told to simultaneously produce a high Q and a low Q.

This produces a "race condition" within the circuit - whichever gate succeeds in changing first will feedback to the other and assert itself. Ideally, both gates are identical and this is "metastable", and the device will be in an undefined state for an indefinite period.

In real life, due to manufacturing methods, one gate will always win, but it's impossible to tell which it will be for a particular device from an assembly line.


The state of $S = R = 1$ is therefore "illegal" and should never be entered.


Latches

The active-HIGH S-R latch is in a stable (latched) condition when both inputs are LOW.

Assume the latch is initially RESET ($Q = 0$) and the inputs are at their inactive level (0). To SET the latch ($Q = 1$), a momentary HIGH signal is applied to the S input while the R remains LOW.

 To RESET the latch ($Q = 0$), a momentary HIGH signal is applied to the R input while the S remains LOW.





An invalid condition in the operation of an active-LOW input S-R latch occurs when LOWs are applied to both S and R at the same time.

As long as the LOW levels are simultaneously held on the inputs, both the Q and \bar{Q} outputs are forced HIGH, thus violating the basic complementary operation of the outputs.

Also, if the LOWs are released simultaneously, both outputs will attempt to go LOW.

Since there is always some small difference in the propagation delay time of the gates, one of the gates will dominate in its transition to the LOW output state.

This, in turn, forces the output of the slower gate to remain HIGH.



In this situation, you cannot reliably predict the next state of the latch.


Latches

The active-LOW \bar{S} - \bar{R} latch is available as the 74LS279A IC.

It features four internal latches with two having two \bar{S} inputs. To SET any of the latches, the \bar{S} line is pulsed low. It is available in several packages.

 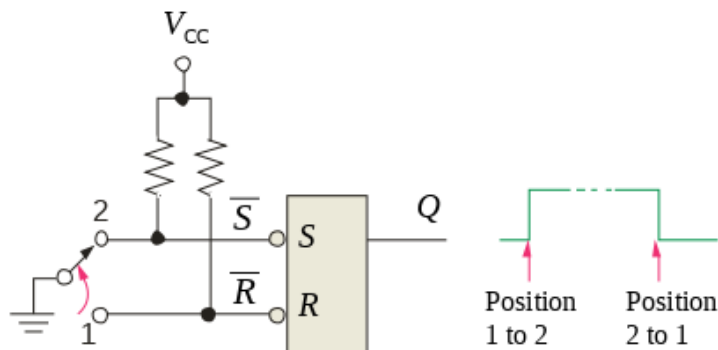\bar{S} - \bar{R} latches are frequently used for switch debounce circuits as shown:



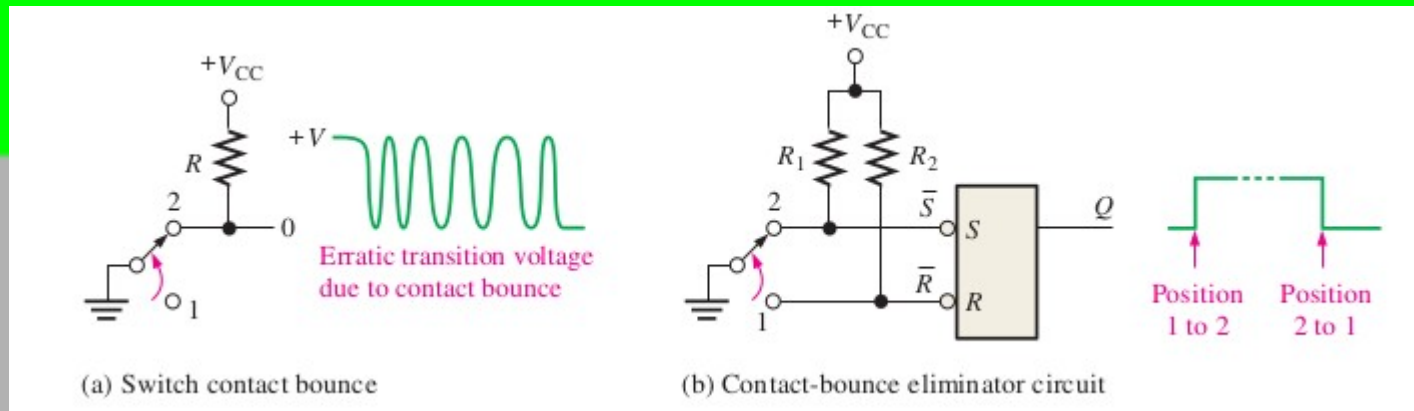

An S-R latch can be used to eliminate the effects of switch bounce.

The switch is normally in position 1, keeping the R input LOW and the latch RESET. When the switch is thrown to position 2, R goes HIGH because of the pull-up resistor to VCC, and S goes LOW on the first contact. Although S remains LOW for only a very short time before the switch bounces, this is sufficient to set the latch. Any further voltage spikes on the S input due to switch bounce do not affect the latch, and it remains SET.

Notice that the Q output of the latch provides a clean transition from LOW to HIGH, thus eliminating the voltage spikes caused by contact bounce.

Similarly, a clean transition from HIGH to LOW is made when the switch is thrown back to position 1.

Latches



A gated latch is a variation on the basic latch.

The gated latch has an additional input, called enable (EN) that must be HIGH in order for the latch to respond to the S and R inputs.

  Example Show the Q output with relation to the input signals.


Assume Q starts LOW.

Solution Keep in mind that S and R are only active when EN is HIGH.



Latches

 The D latch is an variation of the S - R latch but combines the S and R inputs into a single D input as shown:



A simple rule for the D latch is:

Q follows D when the Enable is active.

Latches



The truth table for the D latch summarizes its operation. If EN is LOW, then there is no change in the output and it is latched.

Inputs		Outputs		Comments
D	EN	Q	\bar{Q}	
0	1	0	1	RESET
1	1	1	0	SET
X	0	Q_0	\bar{Q}_0	No change


Latches

  Example

Determine the Q output for the D latch, given the inputs shown.



Notice that the Enable is not active during these times, so the output is latched.



The issue with level triggering is that while the clock level is high, inputs change the outputs. In circuits that have feedback (the outputs are connected back to the inputs) level triggering causes chaos, because the level is wide enough (half a clock cycle) that the output can feed back to the inputs within the same period.

So by the time the well-defined moment occurs when the clock falls and every device is supposed to snapshot and hold its state until the next level, chaos has already occurred and the circuits are in unpredictable states. This is unacceptable.


In sequential circuits, we want the outputs produced in clock period t to only come into consideration for computing the states of clock period $t+1$.

Flip-flops are edge-triggered or edge-sensitive whereas gated latches are level-sensitive

Flip-flops

A flip-flop differs from a latch in the manner it changes states. A flip-flop is a clocked device, in which only the clock edge determines when a new bit is entered.

 The active edge can be positive or negative.



Flip-flops

The truth table for a positive-edge triggered D flip-flop shows an up arrow to remind you that it is sensitive to its D input only on the rising edge of the clock; otherwise it is latched. The truth table for a negative-edge triggered D flip-flop is identical except for the direction of the arrow.


Inputs		Outputs		Comments
D	CLK	Q	\bar{Q}	
1	↑	1	0	SET
0	↑	0	1	RESET

(a) Positive-edge triggered

Inputs		Outputs		Comments
D	CLK	Q	\bar{Q}	
1	↓	1	0	SET
0	↓	0	1	RESET

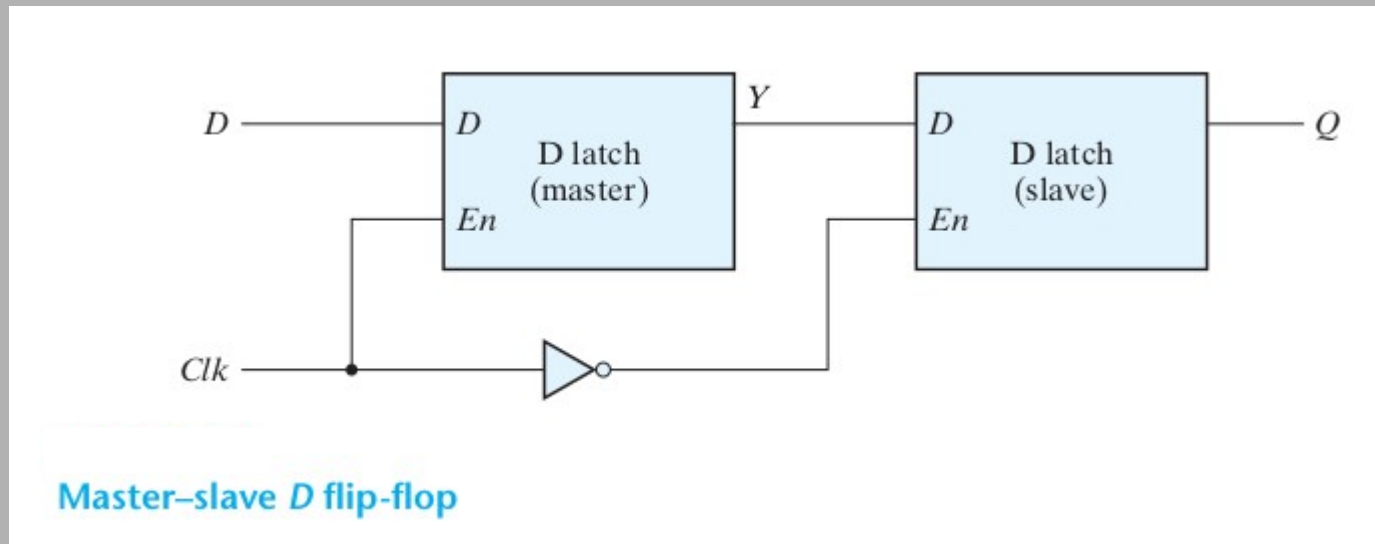
(b) Negative-edge triggered

Thus, a change in the output of the flip-flop can be triggered only by and during the transition of the clock from 1 to 0.




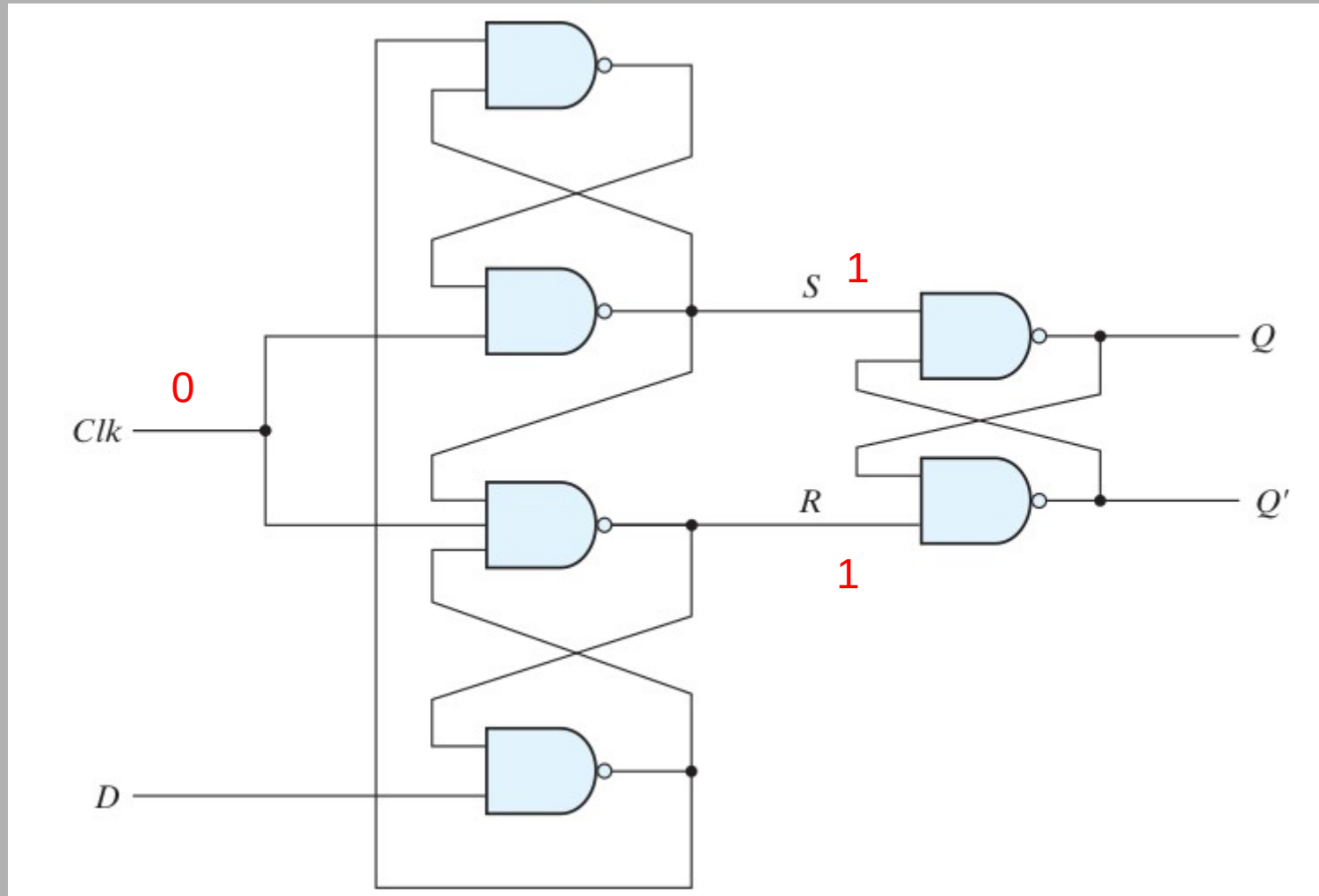- (1) the output may change only once
- (2) a change in the output is triggered by the negative edge of the clock, and
- (3) the change may occur only during the clock's negative level. The value that is produced at the output of the flip-flop is the value that was stored in the master stage immediately before the negative edge occurred.

The advantage of this circuit is that it uses only 6 NAND gates (24 transistors) as opposed to 10 gates (36 transistors)



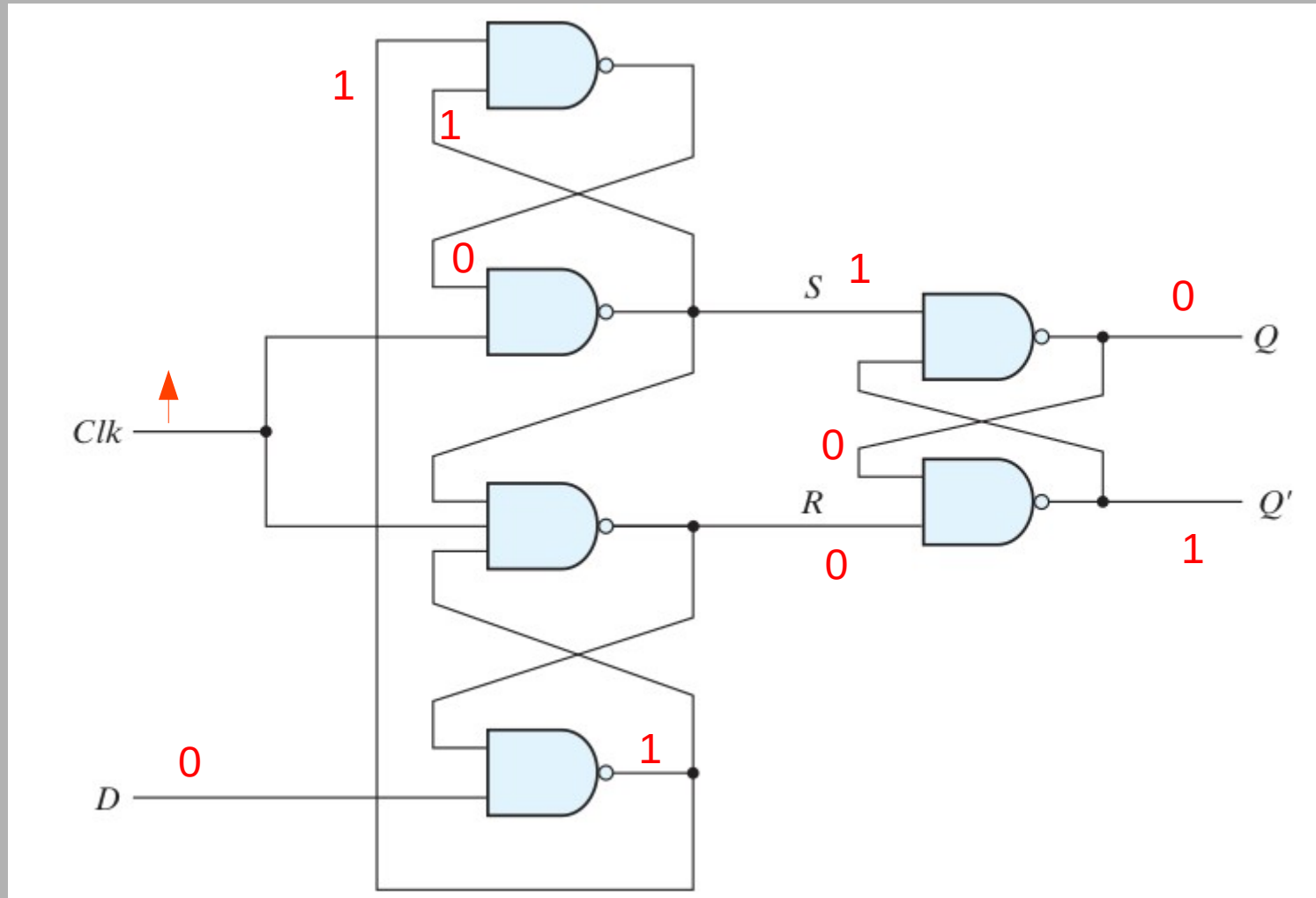
If there is a change in the D input while $\text{Clk} = 1$, terminal R remains at 0 because Q is 0. Thus, the flip-flop is locked out and is unresponsive to further changes in the input.



Flip-flops

The J-K flip-flop is more versatile than the D flip flop. In addition to the clock input, it has two inputs, labeled J and K . When both J and $K = 1$, the output changes states (toggles) on the active clock edge (in this case, the rising edge).

Inputs			Outputs		Comments
J	K	CLK	Q	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	\bar{Q}_0	Q_0	Toggle

 


Flip-flops

 
Example

Determine the Q output for the J - K flip-flop, given the inputs shown.

Notice that the outputs change on the leading edge of the clock.




Solution

 

Flip-flops

A D-flip-flop does not have a toggle mode like the J-K flip-flop, but you can hardwire a toggle mode by connecting \bar{Q} back to D as shown. This is useful in some counters as you will see

 For example, if Q is LOW, \bar{Q} is HIGH and the flip-flop will toggle on the next clock edge. Because the flip-flop only changes on the active edge, the output will only change once for each clock pulse.




D flip-flop hardwired for a toggle mode

Flip-flops

Synchronous inputs are transferred in the triggering edge of the clock (for example the *D* or *J-K* inputs). Most flip-flops have other inputs that are *asynchronous*, meaning they affect the output independent of the clock.

 Two such inputs are normally labeled preset (*PRE*) and clear (*CLR*). These inputs are usually active LOW. A J-K flip flop with active LOW preset and CLR is shown.





Flip-flops

Example


Determine the Q output for the J - K flip-flop, given the inputs shown.

Solution

 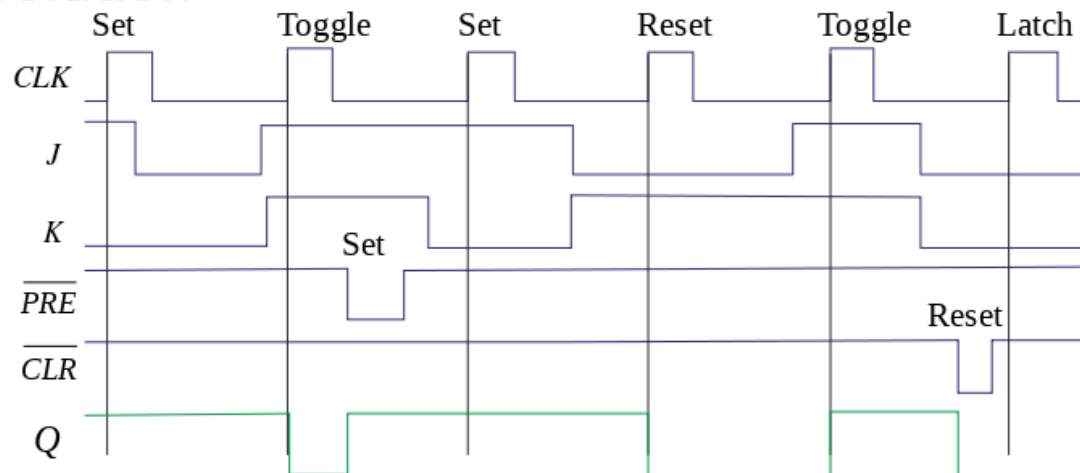

Flip-flop Characteristics


 
Propagation delay time is specified for the rising and falling outputs. It is measured between the 50% level of the clock to the 50% level of the output transition.



The typical propagation delay time for the 74AHC family (CMOS) is 4 ns. Even faster logic is available for specialized applications.

Flip-flop Characteristics

  
Another **propagation delay time** specification is the time required for an *asynchronous* input to cause a change in the output. Again it is measured from the 50% levels. The 74AHC family has specified delay times under 5 ns.




Flip-flop Characteristics

Set-up time and **hold time** are times required before and after the clock transition that data must be present to be reliably clocked into the flip-flop.

 Setup time is the minimum time for the data to be present *before* the clock.



 Hold time is the minimum time for the data to *remain* after the clock.



Maximum Clock Frequency

The maximum clock frequency (f_{\max}) is the highest rate at which a flip-flop can be reliably triggered. At clock frequencies above the maximum, the flip-flop would be unable to respond quickly enough, and its operation would be impaired.

Pulse Widths

Minimum pulse widths (t_w) for reliable operation are usually specified by the manufacturer for the clock, preset, and clear inputs. Typically, the clock is specified by its minimum HIGH time and its minimum LOW time.

Flip-flop Characteristics

Other specifications include maximum clock frequency, minimum pulse widths for various inputs, and power dissipation. The power dissipation is the product of the supply voltage and the average current required.

A useful comparison between logic families is the **speed-power product** which uses two of the specifications discussed: the average propagation delay and the average power dissipation. The unit is energy.

Example What is the speed-power product for 74AHC74A?

Solution the average propagation delay is 4.6 ns.
The quiescent power dissipated is 1.1 mW. Therefore, the speed-power product is **5 pJ**


Comparison of operating parameters for four IC families of flip-flops of the same type at 25°C.

Parameter	CMOS		Bipolar (TTL)	
	74HC74A	74AHC74	74LS74A	74F74
t_{PHL} (CLK to Q)	17 ns	4.6 ns	40 ns	6.8 ns
t_{PLH} (CLK to Q)	17 ns	4.6 ns	25 ns	8.0 ns
$t_{PHL}(\overline{CLR}$ to Q)	18 ns	4.8 ns	40 ns	9.0 ns
$t_{PLH}(\overline{PRE}$ to Q)	18 ns	4.8 ns	25 ns	6.1 ns
t_s (set-up time)	14 ns	5.0 ns	20 ns	2.0 ns
t_h (hold time)	3.0 ns	0.5 ns	5 ns	1.0 ns
t_W (CLK HIGH)	10 ns	5.0 ns	25 ns	4.0 ns
t_W (CLK LOW)	10 ns	5.0 ns	25 ns	5.0 ns
$t_W(\overline{CLR}/\overline{PRE})$	10 ns	5.0 ns	25 ns	4.0 ns
f_{max}	35 MHz	170 MHz	25 MHz	100 MHz
Power, quiescent	0.012 mW	1.1 mW		
Power, 50% duty cycle			44 mW	88 mW

Flip-flop Applications

Principal flip-flop applications are for temporary data storage, as frequency dividers, and in counters

 Typically, for **data storage** applications, a group of flip-flops are connected to parallel data lines and clocked together. Data is stored until the next clock pulse.




Flip-flop Applications


For **frequency division**, it is simple to use a flip-flop in the toggle mode or to chain a series of toggle flip flops to continue to divide by two.

 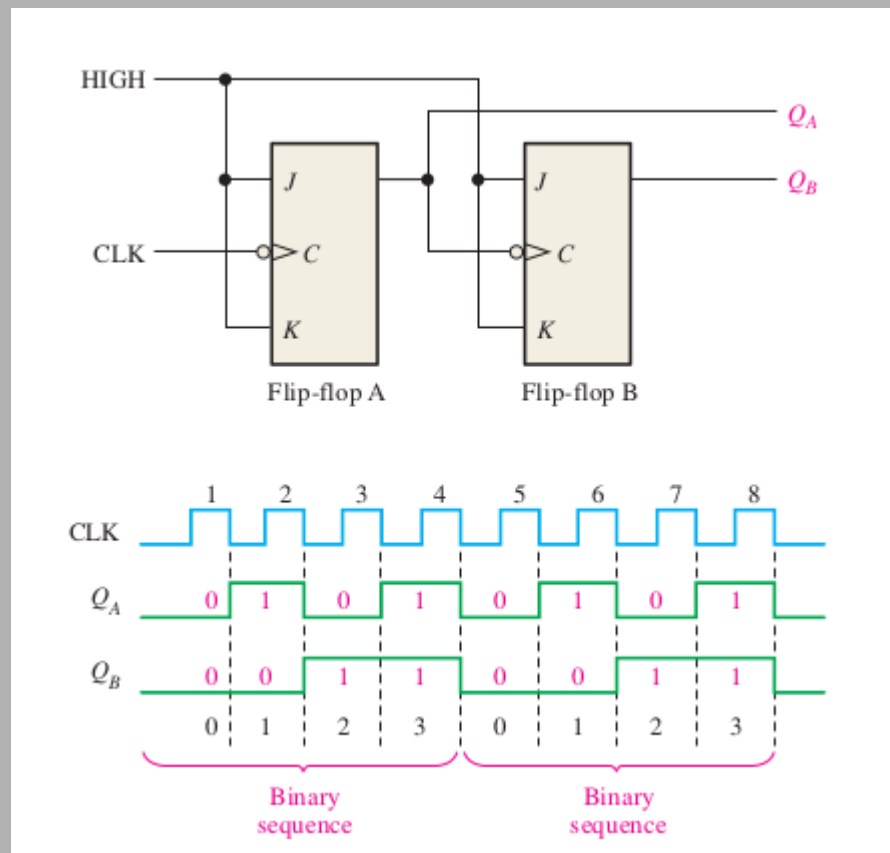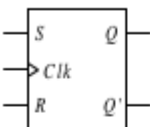

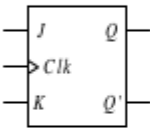
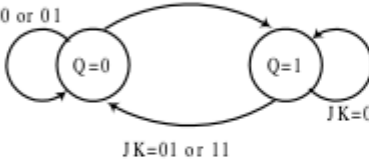
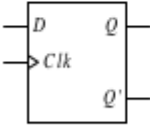
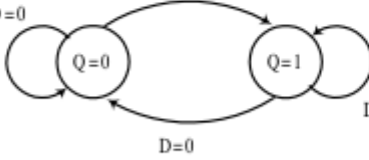
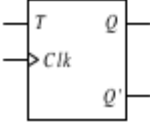
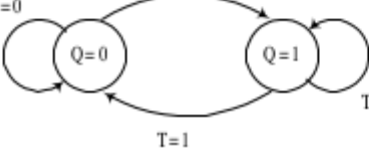
One flip-flop will divide f_{in} by 2, two flip-flops will divide f_{in} by 4 (and so on). A side benefit of frequency division is that the output has an exact 50% duty cycle.

Waveforms:



J-K flip-flops used to generate a binary count sequence (00, 01, 10, 11).
Two repetitions are shown.



Name / Symbol	Characteristic (Truth) Table	State Diagram / Characteristic Equations	Excitation Table																																																								
SR 	<table><tr><th>S</th><th>R</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>×</td></tr><tr><td>1</td><td>1</td><td>1</td><td>×</td></tr></table>	S	R	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	×	1	1	1	×	<p>SR=10</p> <p>SR=00 or 01</p>  <p>SR=00 or 10</p> <p>SR=01</p> <p>$Q_{next} = S + R'Q$</p> <p>$SR = 0$</p>	<table><tr><th>Q</th><th>Q_{next}</th><th>S</th><th>R</th></tr><tr><td>0</td><td>0</td><td>0</td><td>×</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>×</td><td>0</td></tr></table>	Q	Q _{next}	S	R	0	0	0	×	0	1	1	0	1	0	0	1	1	1	×	0
S	R	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	×																																																								
1	1	1	×																																																								
Q	Q _{next}	S	R																																																								
0	0	0	×																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	1	×	0																																																								
JK 	<table><tr><th>J</th><th>K</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	J	K	Q	Q _{next}	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	<p>JK=10 or 11</p> <p>JK=00 or 01</p>  <p>JK=00 or 10</p> <p>JK=01 or 11</p> <p>$Q_{next} = J'K'Q + JK' + JKQ'$</p> <p>$= J'K'Q + JK'Q + JK'Q' + JKQ'$</p> <p>$= K'Q(J'+J) + JQ'(K'+K)$</p> <p>$= K'Q + JQ'$</p>	<table><tr><th>Q</th><th>Q_{next}</th><th>J</th><th>K</th></tr><tr><td>0</td><td>0</td><td>0</td><td>×</td></tr><tr><td>0</td><td>1</td><td>1</td><td>×</td></tr><tr><td>1</td><td>0</td><td>×</td><td>1</td></tr><tr><td>1</td><td>1</td><td>×</td><td>0</td></tr></table>	Q	Q _{next}	J	K	0	0	0	×	0	1	1	×	1	0	×	1	1	1	×	0
J	K	Q	Q _{next}																																																								
0	0	0	0																																																								
0	0	1	1																																																								
0	1	0	0																																																								
0	1	1	0																																																								
1	0	0	1																																																								
1	0	1	1																																																								
1	1	0	1																																																								
1	1	1	0																																																								
Q	Q _{next}	J	K																																																								
0	0	0	×																																																								
0	1	1	×																																																								
1	0	×	1																																																								
1	1	×	0																																																								
D 	<table><tr><th>D</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>×</td><td>0</td></tr><tr><td>1</td><td>×</td><td>1</td></tr></table>	D	Q	Q _{next}	0	×	0	1	×	1	<p>D=1</p> <p>D=0</p>  <p>D=1</p> <p>D=0</p> <p>$Q_{next} = D$</p>	<table><tr><th>Q</th><th>Q_{next}</th><th>D</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Q	Q _{next}	D	0	0	0	0	1	1	1	0	0	1	1	1																																
D	Q	Q _{next}																																																									
0	×	0																																																									
1	×	1																																																									
Q	Q _{next}	D																																																									
0	0	0																																																									
0	1	1																																																									
1	0	0																																																									
1	1	1																																																									
T 	<table><tr><th>T</th><th>Q</th><th>Q_{next}</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	T	Q	Q _{next}	0	0	0	0	1	1	1	0	1	1	1	0	<p>T=1</p> <p>T=0</p>  <p>T=0</p> <p>T=1</p> <p>$Q_{next} = TQ' + T'Q = T \oplus Q$</p>	<table><tr><th>Q</th><th>Q_{next}</th><th>T</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	Q	Q _{next}	T	0	0	0	0	1	1	1	0	1	1	1	0																										
T	Q	Q _{next}																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									
Q	Q _{next}	T																																																									
0	0	0																																																									
0	1	1																																																									
1	0	1																																																									
1	1	0																																																									

- Latch*** A bistable digital circuit used for storing a bit.
- Bistable*** Having two stable states. Latches and flip-flops are bistable multivibrators.
- Clock*** A triggering input of a flip-flop.
- D flip-flop*** A type of bistable multivibrator in which the output assumes the state of the *D* input on the triggering edge of a clock pulse.
- J-K flip-flop*** A type of flip-flop that can operate in the SET, RESET, no-change, and toggle modes.

Propagation delay time The interval of time required after an input signal has been applied for the resulting output signal to change.

Set-up time The time interval required for the input levels to be on a digital circuit.

Hold time The time interval required for the input levels to remain steady to a flip-flop after the triggering edge in order to reliably activate the device.