

# Digital Logic Design Exercise

## Boolean Algebra and Logic Simplification

Using Boolean Algebra, simplify the following expressions using a step by step approach where only one simplification is made per step. Identify the specific Rule or Law used each time.

1.  $AB + A(B + C) + B(B + C)$

2.  $[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$

3.  $\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$

4.  $\overline{AB + AC} + \bar{A}\bar{B}C$

Implement the following expressions as stated with the appropriate logic gates. Then implement the simplified expression and compare the number of gates.

5.  $A + AB + A\bar{B}C$

6.  $(\bar{A} + B)C + ABC$

7.  $A\bar{B}C(BD + CDE) + A\bar{C}$